

Inductor Selection for SEPIC Designs

The SEPIC (single-ended primary inductance converter) in an increasingly popular topology, particularly in battery powered applications, as the input voltage can be higher or lower than the output voltage. This presents obvious design advantages but for many engineers the circuit operation and component selection is a mystery, for those that understand the basics the addition of a coupled inductor is an added complication. This article looks at the operation of the SEPIC and compares the design procedure for two single winding inductors with a coupled inductor approach.

Basic Operation

Figure 1 shows the simple circuit diagram for a SEPIC, during the switch (SW) ON time the voltage across both inductors is equal to V_{in} . This is obvious for L1, however it is not so clear for L2. In order to understand this we first need to look at the voltage across C_p , neglecting ripple voltage, this voltage is constantly at the value of V_{in} . The simplest way to see this is when the circuit is at equilibrium, under these conditions there is no DC voltage across L1 or L2, so one side of the capacitor is at V_{in} and the other at zero volts.

When the switch is ON capacitor C_p is connected in parallel with L2, hence the voltage across L2 is the same as the capacitor voltage, $-V_{in}$. This in turn means that diode D1 is reverse bias and the load current is being supplied by capacitor C_{out} . During this period energy is being stored in L1 from the input and in L2 from C_p .

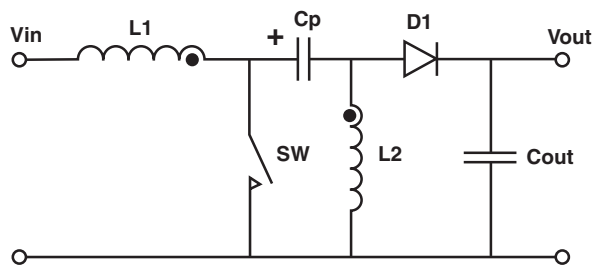


Figure 1 - Simple SEPIC Circuit

When the switch turns off the current in L1 continues to flow through C_p , D1 and into C_{out} and the load recharging C_p ready for the next cycle. The current in L2 also flows into C_{out} and the load, ensuring that C_{out} is recharged ready for the next cycle.

During this period the voltage across both L1 and L2 is equal to V_{out} , once again this is fairly clear for L2 but not so for L1. However we already know that the voltage across C_p is equal to V_{in} and that the voltage on L2 is

equal to V_{out} , in order for this to be true the voltage at the node of C_p and L1 must be $V_{in} + V_{out}$. This in turn means that the voltage across L1 is $(V_{in} + V_{out}) - V_{in} = V_{out}$.

Inductor Selection

First, let us look at the selection of two separate inductors for L1 and L2 in the following example:

Input voltage (V_{in}) – 2.8V – 4.5V
Output (V_{out} & I_{out}) – 3.3V, 1A
Switching Frequency (F_s) – 250kHz
Efficiency - 90%

First we need to calculate the duty cycle;

$$D = V_{out} / (V_{out} + V_{in})$$

The worst case condition for inductor ripple current is at maximum input voltage so;

$$D = 3.3 / (3.3 + 4.5) = 0.423$$

Normally, the output inductor is sized to ensure that the inductor current is continuous at minimum load and that the output voltage ripple does not affect the circuit that the converter is powering. In this case we will assume a 20% minimum load thus allowing a 40% peak to peak ripple current in the output inductor L2.

Calculating the value of L2;

$$V = L \, di/dt$$

Where V is the voltage applied to the inductor, L in the inductance, di is the inductor peak to peak ripple current and dt is the duration the voltage is applied for. Hence;

$$L = V \cdot dt / di$$

$$dt = 1 / F_s \times D$$

$$dt = 1 / (250 \times 10^3) \times 0.423 = 1.69 \, \mu s$$

$V = V_{in}$ during the switch ON time so;

$$L2 = 4.5 \times (1.69 \times 10^{-6} / 0.4)$$

$$L2 = 19 \, \mu H$$

Using the nearest preferred value would lead to the selection of a 22 μH inductor. It is common practice to select the same value for both input and output inductors

in SEPIC designs although when two separate parts are being used it is not essential.

Having selected the inductance value we now need to calculate the required RMS and peak current ratings for both inductors.

For input inductor L1;

$$I_{rms} = (V_{out} \times I_{out}) / (V_{in} \text{ (min)} \times \text{efficiency})$$

$$I_{rms} = (3.3 \times 1) / (2.8 \times 0.9) = 1.31A$$

$$I_{peak} = I_{rms} + (0.5 \times \text{ripple})$$

Although worst case ripple current is at maximum input voltage the peak current is normally highest at the minimum input voltage.

$$I_{ripple} = (V \cdot dt) / L$$

$$I_{ripple} = (2.8 \times 2.2 \times 10^{-6}) / 22 \times 10^{-6} = 0.28A$$

$$I_{peak} = 1.31 + 0.14 = 1.45A$$

So a 22 μ H, 1.31Arms & 1.45Apk rated inductor is required. For example the DR73-220 from Cooper Bussmann's Coiltronics® range, this part is 7.5mm square and 3.5mm high with 1.62Arms and 1.67Apk current ratings.

For the output inductor L2

$$I_{rms} = I_{out} = 1A$$

$$I_{ripple} = (4.5 \times 1.69 \times 10^{-6}) / 22 \times 10^{-6} = 0.346A$$

$$I_{peak} = 1 + 0.173 = 1.173A$$

So a 22 μ H, 1Arms & 1.173Apk rated inductor is required, which for simplicity could be the same DR73-220 inductor used for L1.

Coupled Inductor Selection

When calculating the value for a coupled inductor you need to bear in mind that all the current is effectively flowing in one inductor and that if the two windings are closely coupled the ripple current will be split equally between them. So calculating the inductance value;

$$L = V \cdot dt / di$$

From our earlier example the output ripple current needs to be 0.4Apk-pk, so now we calculate for 0.8A as the

ripple current is split between the two windings

$$L = 4.5 \times (1.69 \times 10^{-6} / 0.8) = 9.5\mu H$$

From this it can be seen that by using a coupled inductor the required inductance is halved. It is also important to note that because the two windings are on the same core they must be the same value. If they are not the voltage across each winding will not be equal and Cp will act as a short circuit to the difference.

Continuing with the example using an inductance value of 10 μ H we now need to calculate the worst case peak current requirement. We already know the RMS current in each winding,

$$\text{Input inductor RMS current} = 1.31A$$

$$\text{Output inductor RMS current} = 1A$$

$$I_{peak} = I_{in} + I_{out} + (0.5 \times I_{ripple})$$

$$I_{ripple} = (2.8 \times 2.2 \times 10^{-6}) / 10 \times 10^{-6} = 0.62A$$

$$I_{peak} = 1.31 + 1 + 0.31 = 2.62A \text{ @ minimum input voltage}$$

So a 10 μ H coupled inductor with 2.31Arms and 2.62Apk current ratings is required, for example the Coiltronics® DRQ74-100. This part has the same 7.5mm square footprint as the DR73-220 that was selected in the example using separate inductors but is 4.35mm high.

Using a coupled inductor takes up less space on the PCB and tends to be lower cost than two separate inductors. It also offers the option to have most of the inductor ripple current flow in either the input or the output. This is achieved by using a winding construction that positions most of the leakage inductance in one winding, this will cause most of the ripple current to appear in the opposite winding. By doing this the need for input filtering can be minimized or the output ripple voltage can be reduced to very low levels when supplying sensitive circuits.

Cooper Bussmann offer a number of coupled inductor options from the Coiltronics® range, including the SDQ and DRQ series of shielded drum inductors and the Econo-Pac and Octa-Pac range of toroid inductors. With inductance values from 0.33 μ H to 1mH and sizes from 5.2mm 2 x 1.2mm high up to 12.5mm 2 x 8mm high Coiltronics® offer one of the broadest ranges of coupled inductor solutions.

Visit us on the Web at www.cooperbussmann.com

1225 Broken Sound Pkwy. Suite F Boca Raton, FL 33487

Tel: +1-561-998-4100 Toll Free: +1-888-414-2645 Fax: +1-561-241-6640

This bulletin is intended to present product design solutions and technical information that will help the end user with design applications. Cooper Electronic Technologies reserves the right, without notice, to change design or construction of any products and to discontinue or limit distribution of any products. Cooper Electronic Technologies also reserves the right to change or update, without notice, any technical information contained in this bulletin. Once a product has been selected, it should be tested by the user in all possible applications.

Life Support Policy: Cooper Electronic Technologies does not authorize the use of any of its products for use in life support devices or systems without the express written approval of an officer of the Company. Life support systems are devices which support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in significant injury to the user.